

## Test 1 Review

- Test will be coding in nature
- Focused on material in parallel interfacing
- Theoretical coding questions will be similar to the HW: e.g. value on port when button is pressed
- No overall design problem related to Keypad
  - Keypad problems similar to the HW
- No full code related to LCD.
  - LCD problem similar to the HW
- Draw a schematic of the problem

### 1. PORTS:

- Port direction is DDRx (x=A,B,C,...)
- PORTx used for output
- PINx is used for input

### 2. LED design

- Port direction is output
- Forward drive:
  - LED is connected to ground
  - Arrow of the LED points to ground
  - output is 1 to turn ON
- Reverse drive:
  - LED is connected to VCC
  - Arrow of the LED points to port
  - output is 0 to turn ON
- Enable can be implemented
  - Replace ground or VCC by output pin
  - Arrow of the LED is used to determine drive direction
  - Forward drive:
    - 2 pins: one for drive, one for enable
    - Drive pin = 1, enable pin = 0
  - Reverse drive:
    - 2 pins: one for drive, one for enable
    - Drive pin = 1, enable pin = 0

### 3. Push button design:

- Input is used to detect button
- PULL UP network:
  - input = 1 when button is OFF, 0 when ON
  - Button must be grounded
  - Ground can be replaced by an enable pin:
    - enable pin = 0 for detect input; 1 to disable
- PULL DOWN network:
  - input = 0 when button is OFF, 1 when ON
  - Button must be connected to VCC
  - VCC can be replaced by an enable pin:
    - enable pin = 1 for detect input; 0 to disable

- Debounce the button read:
  - When activity is detected, wait ~1ms and read again

#### 4. Keypad:

- 4x4 keypad: Use 4 pins for output (activations), 4 pins for reading
- 1x4 keypad: Use 4 pins for output (activations), 1 pins for reading
- 4x1 keypad: Use 1 pin for output (activations), 4 pins for reading
- PULL UP network on inputs (rows):
  - input = 1 when button is OFF, 0 when ON
  - to activate, column = 0
- PULL down network on inputs (rows):
  - input = 0 when button is OFF, 1 when ON
  - to activate , column = 1
- Must activate 1 column at a time, then read inputs
- Must debounce

### Practice Problems:

1. Example of LED problems
  - a. The 8xLEDs are connected to port B is forward drive. No enable is used. Draw schematic.
  - b. Val1 is an array of values. Display each value for 1 sec.
  - c. Same as (a) but Use reverse drive
  - d. Same as (a) but Use enable, port A pin 0.
  - e. Same as (a) but instead of val1 use 8 DIP
  - f. Same as (a) but if val1 is signed, display the absolute value
2. Example of pushbutton problems:
  - a. 4 button connected to 4 pins of port B. Write a function that returns 'A', 'B', 'C', or 'D', when button 3,2,1, or 0 are pressed. Use pullup network and no enable pins. Draw the schematic
  - b. Same as (a) but using pull down network
  - c. Same as (a) but use enable on Port A pin 7.
3. Example of keypad problems:
  - a. 1x4 pad write a functions to return key (A,B,C,D)
  - b. 4x1 pad write a function to return key (A,B,C,D)