

Simple Parallel Interfacing

ENEE 3587

Microp Interfacing

Simple Parallel Interfaces

- ❖ Simple parallel interfaces:
 - Simple input/output devices
 - No interrupts needed
 - Connected to port pins
 - Not using any peripherals
- ❖ Examples:
 - Drive LED's
 - Read push button
 - Read dip switch

Voltage Characteristics

- ❖ Voltage parameters related to electrical compatibility
 - Input high voltage (V_{IH})
 - Input low voltage (V_{IL})
 - Output high voltage (V_{OH})
 - Output low voltage (V_{OL})
- ❖ For device X to drive (i.e. control/provide input to) device Y:
 - V_{OH} of device X $\geq V_{IH}$ of device Y.
 - V_{OL} of device X $\leq V_{IL}$ of device Y
- ❖ In case of miss-matching characteristics we need to condition the signals
 - E.g. use op-amps

Current Characteristics

❖ Current parameters related to electrical compatibility

- Input high current (I_{IH})
- Input low current (I_{IL})
- Output high current (I_{OH})
- Output low current (I_{OL})

❖ Device X **current** driving device Y:

- Current flows out from the device X when the driving voltage is high.
- Current flows into the device X when the driving voltage is low.
- Device X must have enough sourcing (supply current) and sinking (absorb current) capability.

❖ If a device X cannot source or sink enough current, then using buffer device is a common solution.

Mega2560 DC Characteristics

Symbol	Parameter	Condition	Min.	Typ.	Max.	Units
V_{IL}	Input Low Voltage, Except XTAL1 and Reset pin	$V_{CC} = 1.8V - 2.4V$ $V_{CC} = 2.4V - 5.5V$	-0.5 -0.5		$0.2V_{CC}^{(1)}$ $0.3V_{CC}^{(1)}$	V
V_{IL1}	Input Low Voltage, XTAL1 pin	$V_{CC} = 1.8V - 5.5V$	-0.5		$0.1V_{CC}^{(1)}$	
V_{IL2}	Input Low Voltage, RESET pin	$V_{CC} = 1.8V - 5.5V$	-0.5		$0.1V_{CC}^{(1)}$	
V_{IH}	Input High Voltage, Except XTAL1 and RESET pins	$V_{CC} = 1.8V - 2.4V$ $V_{CC} = 2.4V - 5.5V$	$0.7V_{CC}^{(2)}$ $0.6V_{CC}^{(2)}$		$V_{CC} + 0.5$ $V_{CC} + 0.5$	
V_{IH1}	Input High Voltage, XTAL1 pin	$V_{CC} = 1.8V - 2.4V$ $V_{CC} = 2.4V - 5.5V$	$0.8V_{CC}^{(2)}$ $0.7V_{CC}^{(2)}$		$V_{CC} + 0.5$ $V_{CC} + 0.5$	
V_{IH2}	Input High Voltage, RESET pin	$V_{CC} = 1.8V - 5.5V$	$0.9V_{CC}^{(2)}$		$V_{CC} + 0.5$	
V_{OL}	Output Low Voltage ⁽³⁾ , Except RESET pin	$I_{OL} = 20mA, V_{CC} = 5V$ $I_{OL} = 10mA, V_{CC} = 3V$			0.9 0.6	
V_{OH}	Output High Voltage ⁽⁴⁾ , Except RESET pin	$I_{OH} = -20mA, V_{CC} = 5V$ $I_{OH} = -10mA, V_{CC} = 3V$	4.2 2.3			μA
I_{IL}	Input Leakage Current I/O Pin	$V_{CC} = 5.5V$, pin low (absolute value)			1	
I_{IH}	Input Leakage Current I/O Pin	$V_{CC} = 5.5V$, pin high (absolute value)			1	$k\Omega$
R_{RST}	Reset Pull-up Resistor		30		60	
R_{PU}	I/O Pin Pull-up Resistor		20		50	

Symbol	Parameter	Condition	Min.	Typ.	Max.	Units
I_{CC}	Power Supply Current ⁽⁵⁾	Active 1MHz, $V_{CC} = 2V$ (ATmega640/1280/2560/1V)		0.5	0.8	mA
		Active 4MHz, $V_{CC} = 3V$ (ATmega640/1280/2560/1L)		3.2	5	
		Active 8MHz, $V_{CC} = 5V$ (ATmega640/1280/1281/2560/2561)		10	14	
		Idle 1MHz, $V_{CC} = 2V$ (ATmega640/1280/2560/1V)		0.14	0.22	
		Idle 4MHz, $V_{CC} = 3V$ (ATmega640/1280/2560/1L)		0.7	1.1	
		Idle 8MHz, $V_{CC} = 5V$ (ATmega640/1280/1281/2560/2561)		2.7	4	
	Power-down mode	WDT enabled, $V_{CC} = 3V$		<5	15	μA
		WDT disabled, $V_{CC} = 3V$		<1	7.5	
V_{ACIO}	Analog Comparator Input Offset Voltage	$V_{CC} = 5V$ $V_{in} = V_{CC}/2$		<10	40	mV
I_{ACLK}	Analog Comparator Input Leakage Current	$V_{CC} = 5V$ $V_{in} = V_{CC}/2$	-50		50	nA
t_{ACID}	Analog Comparator Propagation Delay	$V_{CC} = 2.7V$ $V_{CC} = 4.0V$		750 500		ns

Input and output voltage levels of common logic families

Logic family	VCC	V _{IH}	V _{OH}	V _{IL}	V _{OL}
S ⁴	5 V	2 V	3.0~3.4 V ¹	0.8 V	0.4~0.5 V ²
LS ⁴	5 V	2 V	3.0~3.4 V ¹	0.8 V	0.4~0.5 V ²
AS ⁴	5 V	2 V	3.0~3.4 V ¹	0.8 V	0.35 V
F ⁴	5 V	2 V	3.4 V	0.8 V	0.3 V
HC ³	5 V	3.5 V	4.9 V	1.5 V	0.1 V
HCT ³	5 V	3.5 V	4.9 V	1.5 V	0.1 V
ACT ³	5 V	2 V	4.9 V	0.8 V	0.1 V
ABT ⁵	5 V	2 V	3 V	0.8 V	0.55 V
BCT ⁵	5 V	2 V	3.3 V	0.8 V	0.42 V
FCT ⁵	5 V	2 V	2.4 V	0.8 V	0.55 V

Notes.

1. V_{OH} value will get lower when output current is larger.
2. V_{OL} value will get higher when output current is larger. The V_{OL} values of different logic gates are slightly different.
3. HC, HCT, ACT are based on the CMOS technology.
4. S, LS, AS and F logic families are based on the bipolar technology.
5. ABT, BCT, and FCT are using the Bi-CMOS technology.

Current capabilities of common logic families ¹




Logic family	VCC	I_{IH}	I_{IL}	I_{OH}	I_{OL}
S	5 V	50mA	1.0 mA	1 mA	20 mA
LS	5 V	20mA	0.2 mA	15 mA	24 mA
AS	5 V	20mA	0.5 mA	15 mA	64 mA
F	5 V	20mA	0.5 mA	1 mA	20 mA
HC ³	5 V	1 mA	1 mA	25 mA	25 mA
HCT ³	5 V	1 mA	1 mA	25 mA	25 mA
ACT ³	5 V	1 mA	1 mA	24 mA	24 mA
ABT ³	5 V	1 mA	1 mA	32 mA	64 MA
BCT	5 V	20mA	1 mA	15 mA	64 mA
FCT ³	5 V	1 mA	1 mA	15 mA	64 mA

Notes.

   1. Values are based on the 74xx244 of Texas Instrument (xx is the technology name: S, LS, AS, F, ... etc.)
2. The values for I_{IH} and I_{IL} are input leakage currents.

Interfacing with LED Devices

- ❖ Circuit (a) and (b) are recommended for LEDs that need only small current to light (1~2mA).
- ❖ Circuit (c) is recommended for LEDs that need larger current to light.
- ❖ Current limiting resistors should be 1.5k-2k Ω .




GPIO Programming for LEDs

❖ Design Process:

- Choose a port/pin to connect the LED to.
- Determine LED type: forward vs inverse driven
 - Pin = HI for ON vs Pin = LO for ON
- Set DDR register of the pin to output
- Set/Clear pin using PORT register

❖ Example: Use pin 7 of port B to control direct driven LED
 
```
DDRB  = 0x80; //output on pin7
PORTB = 0x80; //portb_pin7 = HI
```




Driving a 7-Segment Displays

- ❖ Not advisable to connect without a buffer chip when other IOs are connected
- ❖ Octal buffer chip: 74HC244 provides 8 buffered lines.
 - $V_{OH} = 5V$
 - Use 300Ω to provide drive current of 10mA

- ❖ 7 segments: a-g
 - Dot is a typical 8th LED

❖ 2 Variations

 - Common Cathode:
 - All LEDs are grounded
 - Send “1” to turn LED on
- Common Anode:
 - All LEDs are connected to Vcc
 - Send a “0” to turn LED on



Common Cathode 7SD Table

BCD digit	Segments						
	a	b	c	d	e	f	g
0	1	1	1	1	1	1	0
1	0	1	1	0	0	0	0
2	1	1	0	1	1	0	1
3	1	1	1	1	0	0	1
4	0	1	1	0	0	1	1
5	1	0	1	1	0	1	1
6	1	0	1	1	1	1	1
7	1	1	1	0	0	0	0
8	1	1	1	1	1	1	1
9	1	1	1	1	0	1	1

GPIO Programming for Single 7SD

❖ Design Process:


- Determine if 7SD type: common cathode vs anode
 - Common GND pin vs common VCC pin for LEDs
 - LED on: HI input vs LO input
- Determine PORT/pins connections
 - A min of 7 pins
- Set the DDR register to output
- Convert the table into an array of inputs
- To display digit i, output array[i]

7SDx1 Common Cathode Example 1

```
CHAR SSD[]={0x7e, 0x30, 0x6d, 0x79, ..., 0x7b};
```

```
DDRB = 0x7F;      //PORTB PINS 6-0 OUTPUT
```
 
```
PORTB = SSD[0];   //DISPLAYS “0” ON 7SD
```



Digit	abcdefg	HEX
0	*1111110	0x7E
1	*0110000	0x30
2	*1101101	0x6D
3	*1111001	0x79
4	*0110011	0x33
5	*1011011	0x5B
6	*1011111	0x5F
7	*1110000	0x70
8	*1111111	0x7F
9	*1111011	0x7B

7SDx1 Common Cathode Example 2

- ❖ Using the same circuit as before, display 0 to 9 repeatedly on the 7SD. Each digit will be displayed for 1sec.

```
CHAR SSD[]={0x7e, 0x30, 0x6d, 0x79, ..., 0x7b};  
DDRB = 0x7F;          //PORTB PINS 6-0 OUTPUT
```

```
while(1)  
{  for (int i=0; i<10; i++)  
    {  PORTB = SSD[i];          //DISPLAYS i ON 7SD  
        delay1ms(1000);        //delay function  
    }  
}
```

Delay functions

❖ Crude method: Use multiple loops

- One loop to control micro increments (e.g. 1ms, 1us, etc.)
- Micro increments must be converted into count
 - Count is controlled by the number of cycles AND frequency of device
- Another to control macro increments

❖ Calculating delay in seconds: $\text{delay time} = \text{cycles/Clock}$

- For a clock of 16MHz: $1\text{ms} = 16\text{K}/16\text{M}$

❖ Function format:


```
void delay1u(int macro_time)
{
    for(int i=0; i< macro_time; i++)
        for(int j=0; j<micro_count ; j++)
            do_something_useless;
}
```

Multiple 7SD

- ❖ For multiple 7-segmnets display: Commonly scanning is implemented
 - Another port used to select which chip to activate
 - A NPN transistor (2N2222) can be employed to help switch on the chip
 - NPN is connected to common cathode. If the cathode is allowed to connect to ground the chip will light up.
 - A small resistance $200\Omega \sim 1k\Omega$ is needed to drive the transistor into saturation



Multiple 7SDs Diagram

 

Coding Example: Multiple 7SD

- Given: 3x7SDs driven by PB6-PB0. 7SD GND is connected to PA2-PA0. Write a program that will display and repeat the pattern:

123

234

345

456

567

678


789

890

901

012

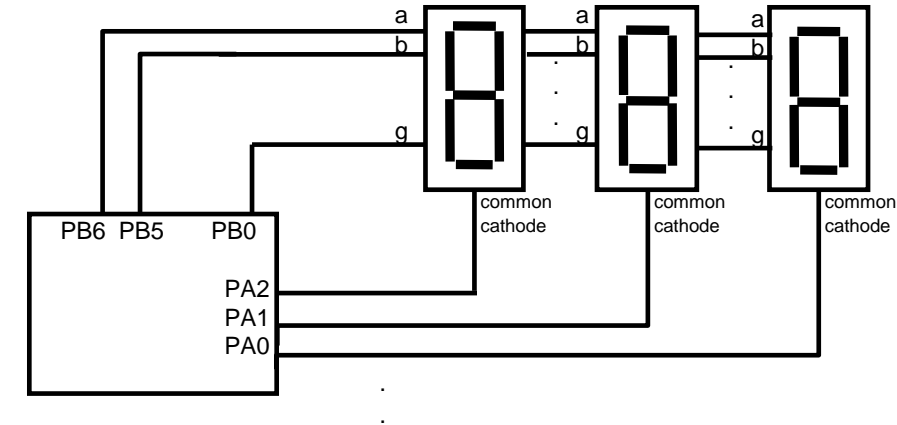Each line of the pattern should display for 1 sec.



Multiple 7SD Example Solution

❖ Idea:

- display each digit for a very short time (10ms-20ms).
- Turn on a 7SD by outputting 0 for its corresponding pin in PORTA
 - Only one 7SD should be ON
 - All others use output 1 (OFF)
- Repeat the line over for 1s.
 - Each 7SD displays for 10ms
 - For 1s repeat: $\text{Repeat } 1\text{s}/\text{delay} = 1000\text{ms}/(30\text{ms}+30\text{ms}+30\text{ms}) \sim 30\text{x}$
 - Must experimentally determine 1s for accurate count
- Move to the next line
 - Start with digit 1
 - Display digit, digit+1, digit+2
 - For next line increment digit

Multiple 7SD Example Algorithm

Create an array for each digit: "1","2","...", "9","0","1","2"

Set the PORTA,B for output

For i = 1 to 10:

//10 lines of patterns

For j = 1 to 30:

//Assume 30x30ms ~ 1s

PORTB = array[i]

PORTA = ~4

//4=b100; ~4= 011; PA2=011

delay1ms(10)

PORTB = array[i+1]

PORTA = ~2

//2=b010; ~2=101; PA1=101

delay1ms(10)

PORTB = array[i+2]


PORTA = ~1

//1=b001; ~1=110; PA0=110

delay1ms(10)

4x Seven Segment Display

 
- ❖ 5643A: common cathode; 5643B: common anode;
- ❖ Segments a,b,c,d,e,f,g: pins 11,7,4,2,1,10,5
- ❖ “Enable” pins for 7SD1,2,3,4: pins 12, 9,8,6
 - Common cathode: GND
 - Common anode: VCC
- ❖ dot segment: pin 3






Interfacing DIP Switches

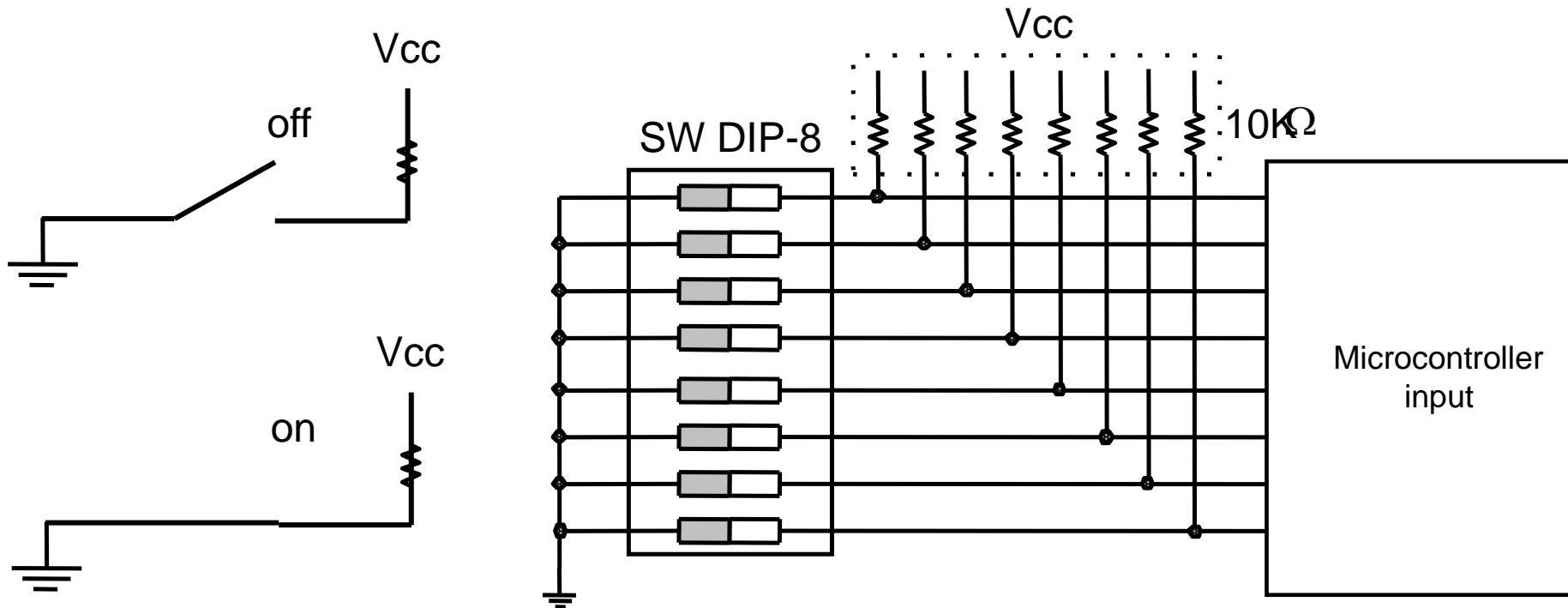- ❖ Dual inline package (DIP): simple input device
- ❖ DIP switches are often used to provide setup information to MCU.
- ❖ For inputs = 5V use 10k Ω to provide 0.5mA input to MCU
- ❖ When in ON position current flows from input to MCU



8xDIP Switch to LEDs

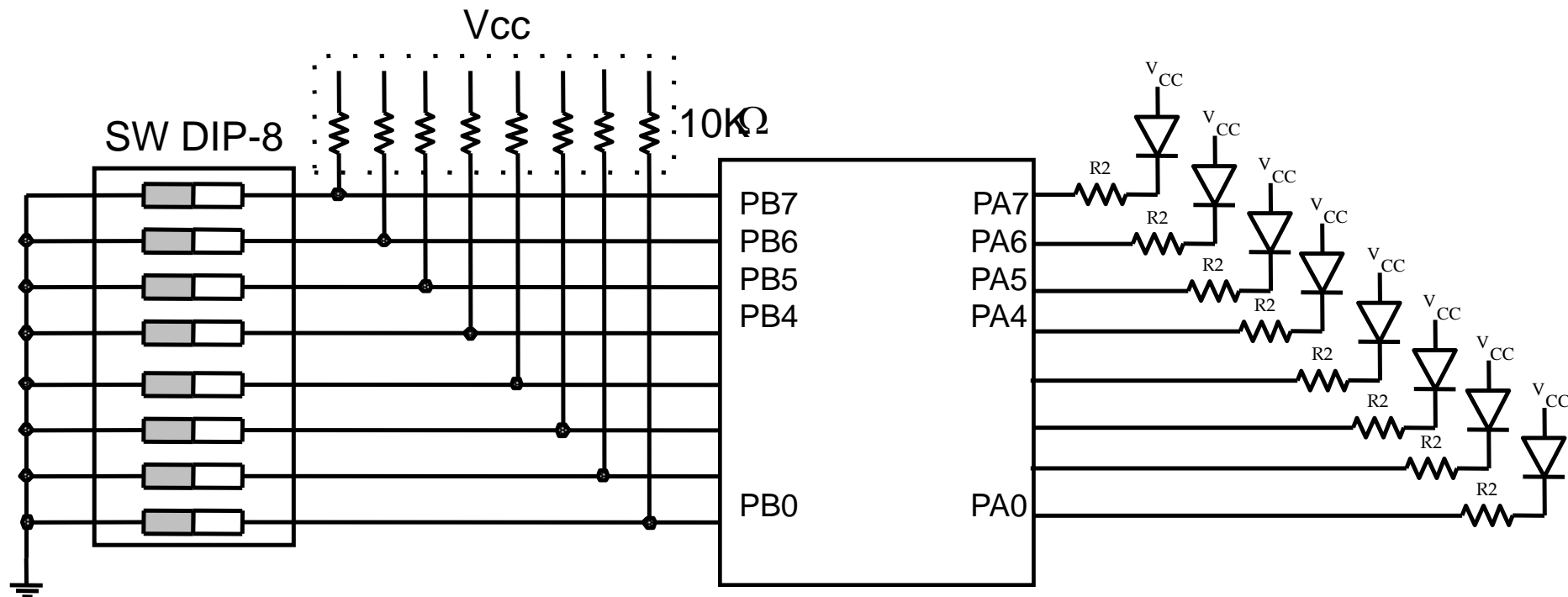- ❖ An 8 input DIP switch is used to turn on 4 LEDs as showt in the diagram. When the switch is ON, turn the corresponding LED ON.



DIP, LED Example Code


- ❖ Configure PORTS for input/output:
 - PORTB must be input; PORTA must be an output port
- ❖ Read PORTB:
 - Use PINB
 - When switch x is ON: $PBx = 0$
- ❖ Turn LEDs ON:
 - When $PAx=0$: LEDx is ON
 - $PORTA = PINB$

```
DDRA = 0xFF;           //output
```

```
DDRB = 0;               //input
```

```
while(1)
```
 
```
    PORTA = PINB;        //BE (NOT) AWARE OF BOUNCE
```





Bounce of a DIP switch
On falling edge $200\mu\text{s}$


Push buttons

- ❖ Do not require advanced synchronization
- ❖ A push-button is switch
 - Can be mechanical, membrane, capacitors, or Hall-effect in construction.
- ❖ Mechanical switches are most popular.
 - Problem: contact bounce.
 - Closing a mechanical switch generates a series of pulses because the switch contacts do not come to rest immediately.
- ❖ Humans cannot type more than 50 keys in a second. Reading the switch more than 50 times a second will read the same key stroke too many times.
 - $1/50 = 0.02\text{s} = 20\text{ms}$


Timing Compatibility

  - ❖ There is no timing problem when driving a peripheral pin that does not contain latches or flip-flops.
- ❖ When driving a latch or flip-flop device, one needs to make sure that the data set up time (t_{SU}) and data hold time (t_{HD}) are both satisfied.
- ❖ Not a big issue with simple devices




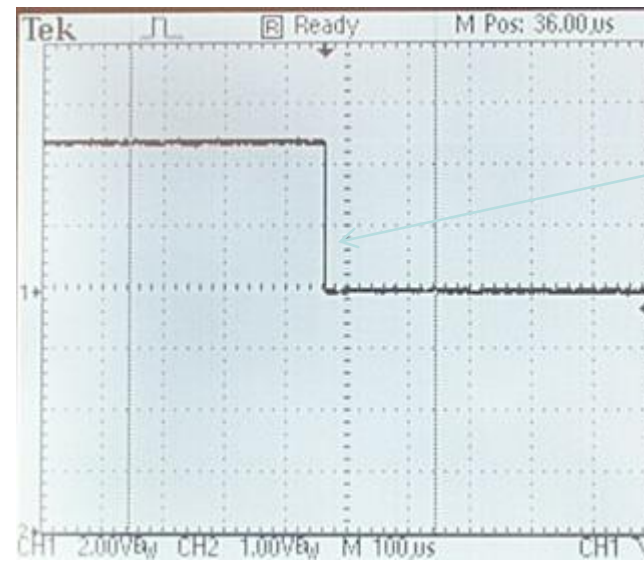

button is pushed

 


button is released 600 μ s bounce

 


button is released 400 μ s bounce

Push Button

 
- ❖ Port must be used as input
- ❖ Strategy:
 - Scan the port for a 0
 - Debounce button
- ❖ Hardware Debouncing Techniques
 - SR latches
 - Non-inverting CMOS gates
 - Integrating debouncer
- ❖ Software debouncing:
 - $<200\mu\text{s}$ delay for DIP; $<1\text{ms}$ delay for pushbutton
 - Adv: cheaper, controllable
 - Disadv.: consumes power (interrupt driven methods less power consumption).




Hardware Debouncing

 

(a) Set-reset latch

 


(b) CMOS gate debouncer

 

(c) Integrating RC circuit debouncer

Figure 7.42 Hardware debouncing techniques

Push Button Example

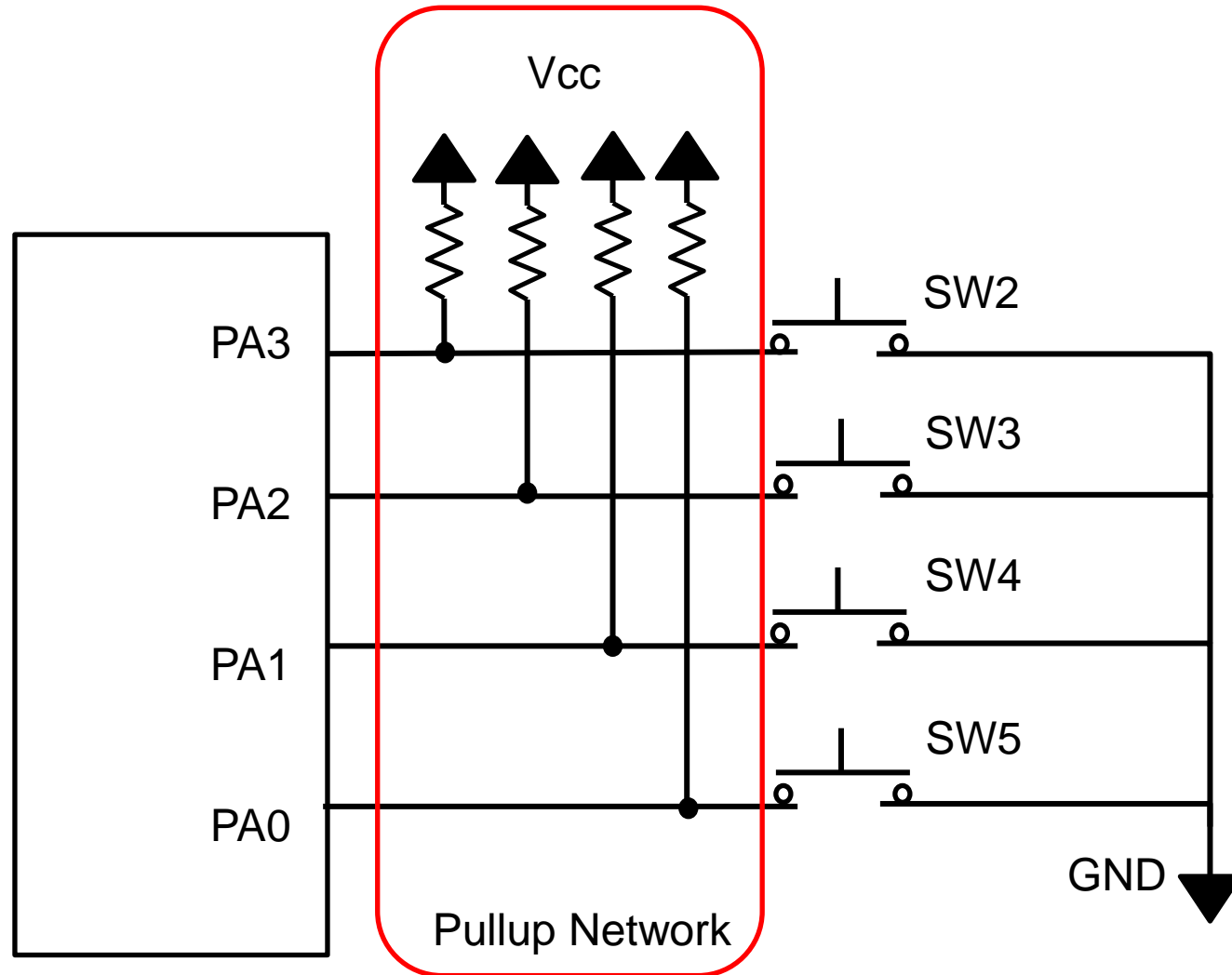

Coding for Push button

- ❖ Set port direction:
 - Read: $\text{DDRx} = 0$
- ❖ Optional: Set the port to PULL-UP (if device PULLUP is used)
 - Enable pullup on the port
- ❖ Read pin
 - Use PINx
 - $\text{PIN} = 0 \Rightarrow$ button is ON
 - If activity is detected, delay 10ms and read again

```
DDRA = 0;
```

```
while(PINA==0x0F);
```


```
delay1ms(10);
```


```
//wait until a button is pressed
```

```
//wait for bounce to be over (debounce)
```

Keypad

 - ❖ Array of pushbutton switches.
 - Typically 12-24 buttons
- ❖ Example: 16 keypad interface
 - Rows configured as input
 - Columns configured as output
 - Pullup network connected to rows
 - To scan a column, output configured to 0
 - When button is not pressed input is 1
 - When button is pressed circuit is connected and input 0



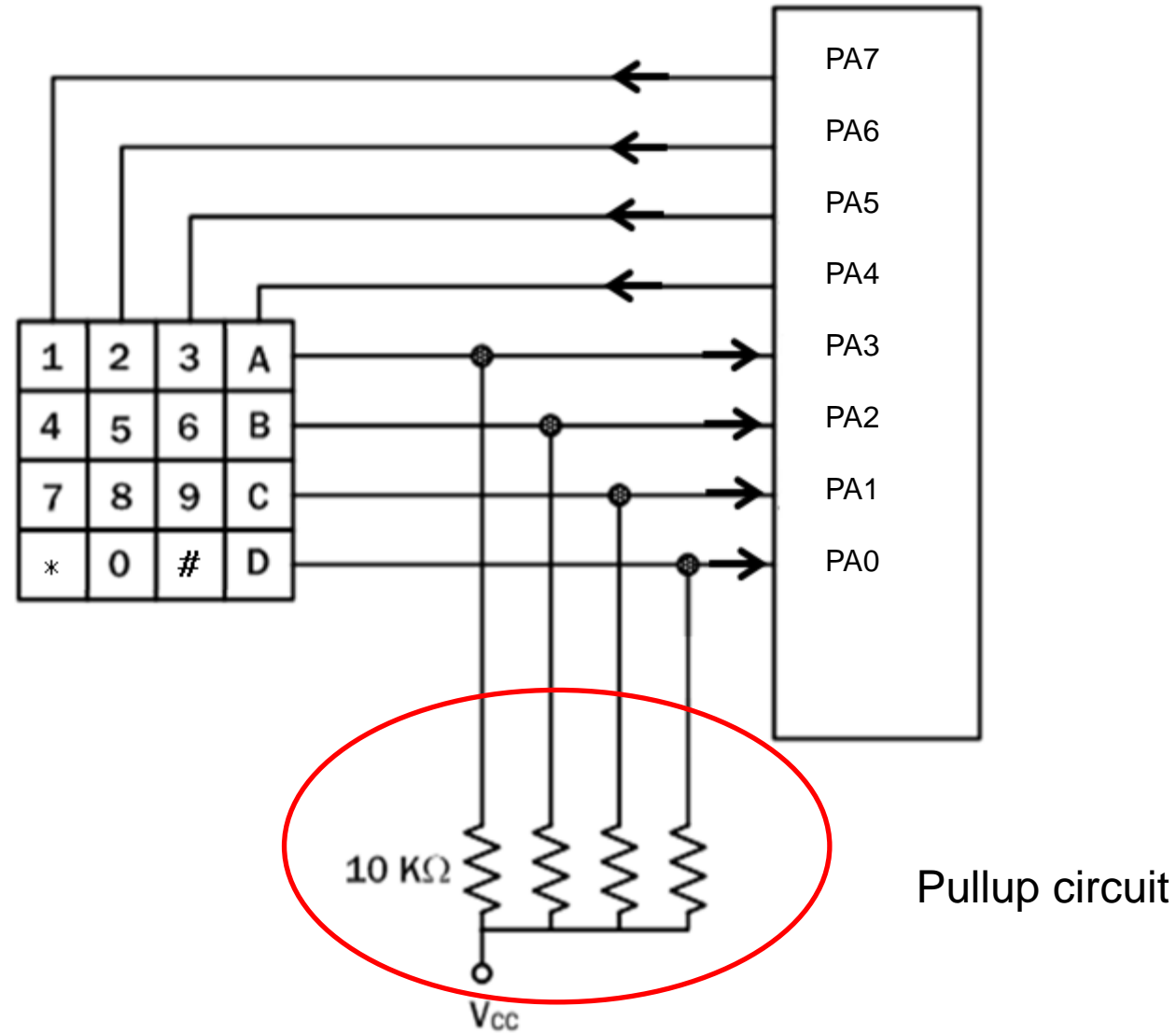

Strategy

1. Use the built in PULLUP Port circuit
2. Enable a single column (send a 0)
3. Read rows (one by one)
4. If key is pressed, delay by 10ms then read again
 - To overcome bouncing
 - Use row, col combination to determine key pressed
 - (col,row) = (0,0) is "1"
 - (col,row) = (4,4) is "D"
 - STOP if key is pressed
5. Enable next column
6. Jump to 2

Code 4x4 Keypad

```

char keypad(void)
{
    char col[] = {0x70, 0xB0, 0xD0, 0xE0}, char key[][] = {{“1”, “2”, “3”, “A”}, ...}
    int r;
    DDRA = 0xF0; //PA7-4: controls columns, PA3-0: input rows
    for (int c = 0; c < 4; c++) // enable each column 1 at a time
    {
        PORTA = col[c];
        if (PINA != 0x0F)
        {
            delay1m(10); //debounce
            switch (PINA & 0x0F)
            {
                case(0b0111): r = 0; break;
                case(0b1011): r = 1; break;
                case(0b1101): r = 2; break;
                case(0b1110): r = 3; break;
                default:
            }
            return (key[r][c]);
        }
    }
}


```

LCD

- ❖ Most common type allows light to pass through when activated
 - activated when a low frequency bipolar signal in the range of 30 Hz to 1KHz is applied to it.
- ❖ Can display characters and graphics.
- ❖ Often sold in a module with LCDs and controller unit built in.

LCM1602A LCD Kit

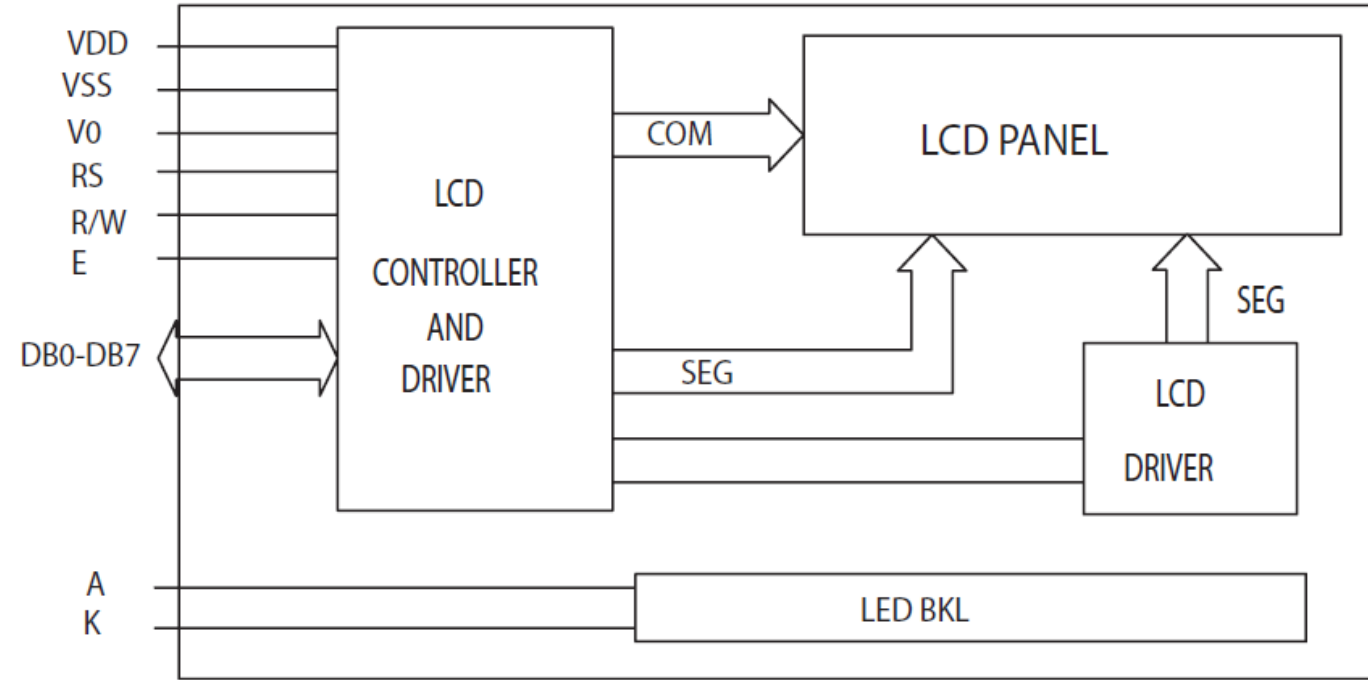- ❖ Display capability: 2 x 16
- ❖ DB0-7 can be used to:
 - Send characters to be display on LCD
 - Send commands to LCD (control cursor, fonts, etc.)
 - Receive status/configuration info from LCD



1-2 Lines LCD

Pin No.	symbol	I/O	Function
1	V_{SS}	-	Power supply (GND)
2	V_{CC}	-	Power supply (+5 V)
3	V_{EE}	-	Contrast adjust
4	RS	I	0 = instruction input, 1 = data input
5	R/\overline{W}	I	0 = write to LCD, 1 = read from LCD
6	E	I	Enable signal
7	DB0	I/O	Data bus line 0
8	DB1	I/O	Data bus line 1
9	DB2	I/O	Data bus line 2
10	DB3	I/O	Data bus line 3
11	DB4	I/O	Data bus line 4
12	DB5	I/O	Data bus line 5
13	DB6	I/O	Data bus line 6
14	DB7	I/O	Data bus line 7

Pins 15,16 control back lighting

3-4 Line LCD

Pin No.	symbol	I/O	Function
1	DB7	I/O	Data bus line 7
2	DB6	I/O	Data bus line 6
3	DB5	I/O	Data bus line 5
4	DB4	I/O	Data bus line 4
5	DB3	I/O	Data bus line 3
6	DB2	I/O	Data bus line 2
7	DB1	I/O	Data bus line 1
8	DB0	I/O	Data bus line 0
9	E1	I	Enable signal row 0 and 1
10	R/ \overline{W}	I	0 = write to LCD, 1 = read from LCD
11	RS	I	0 = instruction input, 1 = data input
12	V _{EE}	-	Contrast adjust
13	V _{SS}	-	Power supply (GND)
14	V _{CC}	-	Power supply (+5 V)
15	E2	I	Enable signal row 2 and 3
16	N.C	-	

Instruction Format

Instruction	Code										Description	Execution Time
	RS	R/ \overline{W}	B7	B6	B5	B4	B3	B2	B1	B0		
Clear display	0	0	0	0	0	0	0	0	0	1	Clears display and returns cursor to the home position (address 0)	1.64 ms
Cursor home	0	0	0	0	0	0	0	0	0	1 *	Returns cursor to home position without changing DDRAM contents. Also returns display being shifted to the original position.	1.64 ms
Entry mode set	0	0	0	0	0	0	0	0	1	I/D S	Sets cursor move direction (I/D); specifies to shift the display (S). These operations are performed during data read/write.	40 μ s
Display on/off control	0	0	0	0	0	0	1	D	C	B	Sets on/off of all display(D), cursor on/off (c), and blink of cursor position character (B).	40 μ s
Cursor/display shift	0	0	0	0	0	1	S/C	R/L	*	*	Sets cursor-move or display-shift (S/C), shift direction (R/L). DDRAM contents remain unchanged.	40 μ s
Function set	0	0	0	0	1	DL	N	F	*	*	Sets interface data length (DL), number of display line (N), and character font (F).	40 μ s
Set CGRAM address	0	0	0	1	CGRAM address						Sets the CGRAM address. CGRAM data are sent and received after this setting.	40 μ s
Set DDRAM address	0	0	1	DDRAM address						Sets the DDRAM address. DDRAM data are sent and received after this setting.	40 μ s	
Read busy flag and address counter	0	1	BF	CGRAM/DDRAM address						Reads busy flag (BF) indicating internal operation being performed and reads CGRAM or DDRAM address counter contents (depending on previous operation).	0 μ s	
Write CGRAM or DDRAM	1	0	write data						Writes data to CGRAM or DDRAM			40 μ s
Read from CGRAM or DDRAM	1	1	read data						Reads data from CGRAM or DDRAM			40 μ s

Instruction Bits

Bit Name	Settings	
I/D	0 = decrement cursor position.	1 = increment cursor position
S	0 = no display shift.	1 = display shift
D	0 = display off	1 = display on
C	0 = cursor off	1 = cursor on
B	0 = cursor blink off	1 = cursor blink on
S/C	0 = move cursor	1 = shift display
R/L	0 = shift left	1 = shift right
DL	0 = 4-bit interface	1 = 8-bit interface
N	0 = 1/8 or 1/11 duty (1 line)	1 = 1/16 duty (2 lines)
F	0 = 5 × 8 dots	1 = 5 × 10 dots
BF	0 = can accept instruction	1 = internal operation in progress

Display Data RAM (DDRAM)

- ❖ 2x16 LCD Module: 2 lines, 16 characters per line
- ❖ Each character location has an address
- ❖ Write in that address a character to display it on the LCD

Display Size	Visible	
	Character Positions	DDRAM Addresses
2 * 16	00..15	0x00..0x0F + 0x40..0x4F
2 * 20	00..19	0x00..0x13 + 0x40..0x53
2 * 24	00..23	0x00..0x17 + 0x40..0x57
2 * 32	00..31	0x00..0x1F + 0x40..0x5F
2 * 40	00..39	0x00..0x27 + 0x40..0x67

ROM/RAM & Registers

❖ CGROM: Character generator ROM

- generates 5x8 or 5x10 character patterns from a 8-bit code

❖ CGRAM: Character generator RAM

- User can rewrite character patterns into CGRAM.
- Up to eight 5x8 patterns or four 5 x10 patterns can be programmed.

❖ Registers: two 8-bit user accessible registers:

- Instruction register (IR): for display control
- Data register (DR): to write and read

RS	R/ \overline{W}	Operation
0	0	IR write as an internal operation (display clear, etc.).
0	1	Read busy flag (DB7) and address counter (DB0 to DB6).
1	0	DR write as an internal operation (DR to DDRAM or CGRAM).
1	1	DR read as an internal operation (DDRAM or CGRAM to DR).

Commands

❖ Clear display

- Writes 0x20 (space character) to all DDRAM locations.
- Sets 0 to the address counter (return cursor to upper left corner of the LCD)
- Sets increment mode

❖ Return Home

- Sets address counter to 0.
- DDRAM contents are not changed.

❖ Entry Mode Set

- Sets incrementing or decrementing of the DDRAM address.
- Controls the shifting (shifts if S bit = 1) of the display

❖ Display On/Off Control

- Turns on/off display
- Turns on/off cursor
- Turns on/off cursor blinking

Cursor vs Shift

- ❖ Cursor can move to right or left
 - Supports different languages
- ❖ Display Shift
 - Entire display shifts

S/C	R/L	Operation
0	0	Shifts the cursor position to the left. (AC is decremented by 1)
0	1	Shifts the cursor position to the right. (AC is incremented by 1)
1	0	Shifts the entire display to the left. The cursor follows the display shift.
1	1	Shifts the entire display to the right. The cursor follows the display shift.

Function Set

- ❖ Sets the interface length (DL bit) to be 4- or 8-bit.
 - Using the 4 bit mode is more complex
 - Data must be sent twice (upper 4 bits are sent first then lower 4 bits)
 - Save on number of used ports/pins
 - Chip starts in 8 bit mode
 - 4 bit mode data transfers on the upper data pins, D4-D7.
- ❖ Selects the number of lines (N bit) to be one or two lines.
- ❖ selects character font (F bit) to be 5x8 or 5x10

Address Regs & Flag

❖ Set CGRAM Address

- This command contains the address to be written into the address counter.

❖ Set DDRAM Address


- This command allows the user to set the starting address to display information.

❖ Read Busy Flag and Address


- This command reads the busy flag and the address counter.
- User can use this command to determine whether the LCD controller is ready to accept another command.
- User can use this command to control where to start displaying information.

Setup

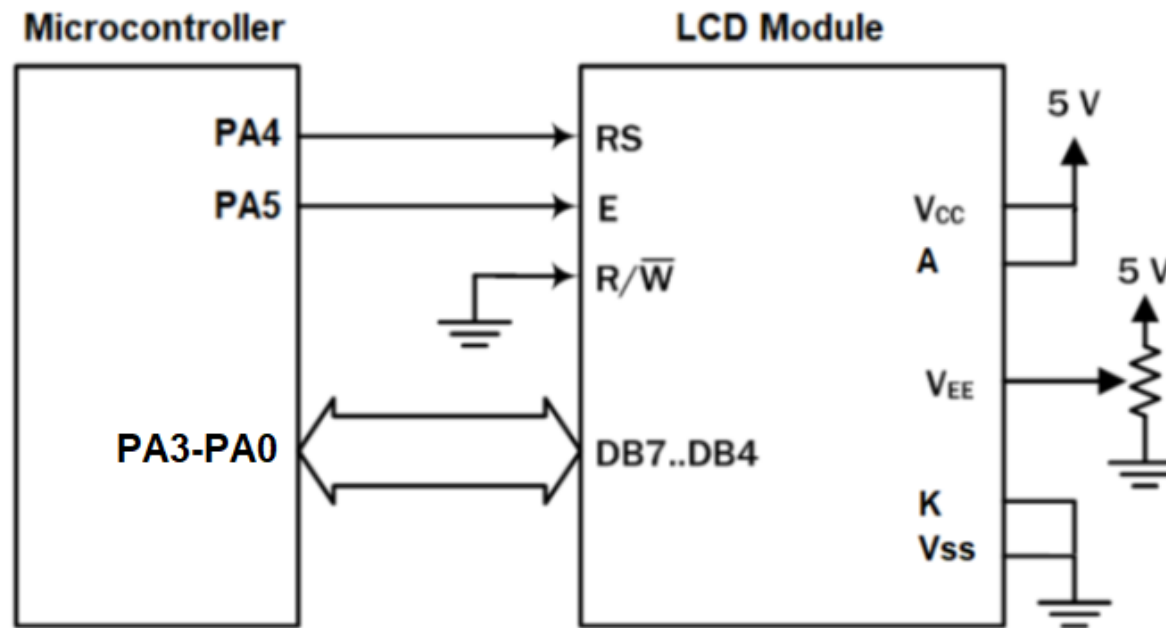- ❖ LCD kit as an I/O device
- ❖ Use 4 bit-interface to save on pins



Timing: Write to LCD

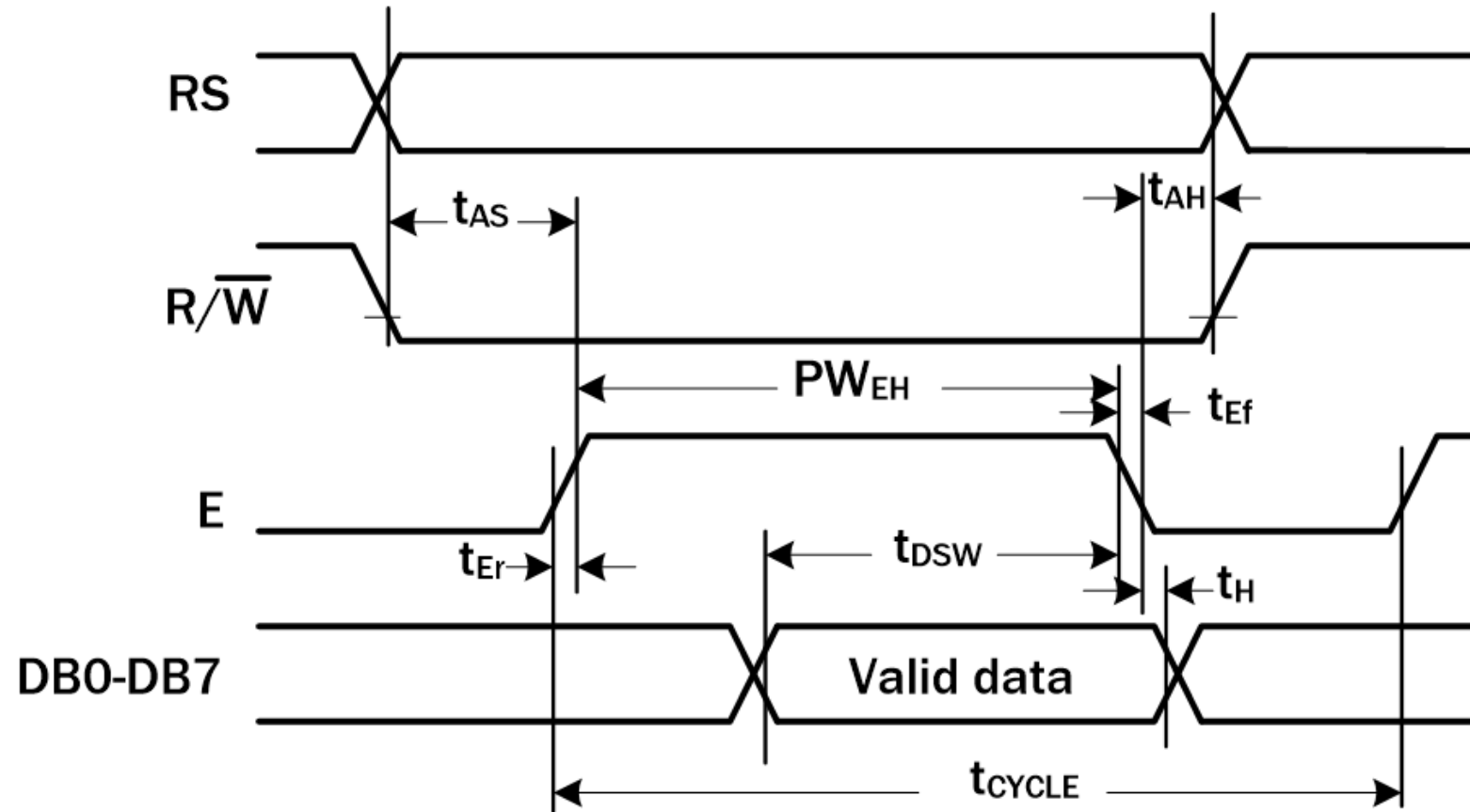

Writing an Instruction to IR

❖ Process:

1. IR instruction write: $RS = 0$
2. Write: $R/W = 0$
 - Based on diagram on previous slide R/W is always 0 => ignore this step
3. Enable input: $E = 1$
4. Output port = instruction
 - Configure IO Port for output before
5. Disable input: $E = 0$

❖ 4-bit interface requires sending the upper bits first, then the lower 4-bits

Writing a Character to LCD

❖ Process:

1. DR Character write: **RS = 1**
2. Write operation: $R/W = 0$
3. Enable input: $E = 1$
4. Output port = instruction
 - Configure IO Port for output before
5. Disable input: $E = 0$

❖ 4-bit interface requires sending the upper bits first, then the lower 4-bits

Coding Examples

❖ Create the following functions:

➤ byte2LCD:

- Send a byte of data to the LCD
- Bytes can be instructions or characters to display
- Bytes are sent in 2 cycles: upper 4 bits, lower 4 bits

➤ setupLCD: sends instructions to the LCD kit:

- Uses byte2LCD
- 4-bit data, 2-line display, 5x8 font
- turn on display, display a blinking cursor
- Set display to display left to right
- Clear display, move cursor home

➤ str2LCD: displays a string on LCD

- Uses byte2LCD

Definitions

```
#define F_CPU 16000000L           // Specify 16MHz frequency
#include <avr/io.h>                // GPIO reg def
#include <util/delay.h>            // delay function

#define LCD_DAT PORTA             // Port A drives LCD data pins, E & RS
#define LCD_DIR DDRA             // Direction of LCD port
#define LCD_E 0x20                // E signal
#define LCD_RS1 0x10             // RS signal: 0 for instr, 1 for char
#define LCD_RS0 0x00             // RS signal: 0 for instr, 1 for char
```

byte2LCD

```

void byte2LCD (char data, char IR_DR)
{
    char temp;
    LCD_DAT = IR_DR;           // set instr or character
    temp = data >> 4;          // get upper 4 bits
    LCD_DAT = IR_DR|LCD_E;     // pull E signal to high
    _delay_ms(5000);
    temp = temp|IR_DR;
    temp = temp|LCD_E;
    LCD_DAT = temp;            // output upper four bits, E, and RS
    _delay_ms(1);              // wait until the send is complete

    LCD_DAT = IR_DR;           // set instr or character
    temp = data & 0x0F;         // keep lower 4 bits
    temp = temp|LCD_E;
    LCD_DAT = IR_DR|LCD_E;     // pull E to high
    temp = temp|IR_DR;
    LCD_DAT = temp;            // output upper four bits, E, and RS
    _delay_ms(1);              // wait until the command is complete
    LCD_DAT = 0;               // pull E clock to low
}

```


setupLCD

```
void setupLCD(void)
{
    LCD_DIR = 0xFF;           // configure LCD_DAT port for output
    byte2LCD(0x28, LCD_RS0);  // set 4-bit data, 2-line display, 5x8 font
    byte2LCD(0x0F, LCD_RS0);  // turn on display, cursor, blinking
    byte2LCD(0x06, LCD_RS0);  // move cursor right
    byte2LCD(0x01, LCD_RS0);  // clear screen, move cursor to home
    _delay_ms(1);             // wait until complete
}
```

str2LCD

```
void str2LCD (char *ptr)
{
    while (*ptr) //ascii-Z strings (null-terminated)
    {
        byte2LCD(*ptr, LCD_RS1);
        ptr++;
    }
}
```

Example Program

```
int main (void)
{
    char *msg1 = "hello world!";
    char *msg2 = "LCD is working!";

    setupLCD();
    str2LCD(msg1);
    byte2LCD(0xC0, LCD_RS0);           // move cursor to 2nd row, 1st column
    str2LCD(msg2);
    while(1);
}
```